

Exercise

A. Multiple-Choice Questions (MCQs)

Tick (✓) the correct answer.

- Which of the following Boolean expressions represents the OR operation?
(a) $A \cdot B$ (b) $A + B$ (c) A (d) $A \oplus B$
- What is the dual of the Boolean expression $A \cdot 0 = 0$?
(a) $A + 1 = 1$ (b) $A + 0 = A$ (c) $A \cdot 1 = A$ (d) $A \cdot 0 = 0$
- Which logic gate gives output "true" only when both inputs are true?
(a) OR gate (b) AND gate (c) XOR gate (d) NOT gate
- In a half-adder circuit, the carry is generated by which operation?
(a) XOR operation (b) AND operation (c) OR operation (d) NOT operation
- What is the decimal equivalent of binary number 1101?
(a) 11 (b) 12 (c) 13 (d) 14

B. Short Questions

- Define a Boolean function and give an example.**
A Boolean function is an expression made using Boolean variables and logical operations like AND, OR, and NOT.
Example: $F = A + B$
- What is the significance of the truth table in digital logic?**
A truth table shows all possible input values and their corresponding output. It helps understand how a logic gate or circuit behaves.
- Explain the difference between analog and digital signals.**
Analog signals are continuous and vary smoothly.
Digital signals are in discrete steps, usually only 0 and 1.
- Describe the function of a NOT gate with its truth table.**
A NOT gate inverts the input. If input is 1, output is 0 and vice versa.

Input	Output
0	1
1	0
- What is the purpose of a Karnaugh map in simplifying Boolean expressions?**
A Karnaugh Map (K-Map) is used to simplify Boolean expressions easily by grouping adjacent 1s in a truth table format.

C. Long Questions (Detailed Answers)

1. **Explain the usage of Boolean functions in computers.**

Boolean functions are used in computers for decision-making, controlling circuits, building logic gates, and simplifying complex logic in programming and hardware.

2. **Describe how to construct a truth table for a Boolean expression with an example.**

List all possible inputs (like A, B), then calculate the output for each.

Example for $F = A + B$:

A	B	$F = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

3. **Describe the concept of duality in Boolean algebra and give an example.**

Duality means replacing + with $\cdot$ and 0 with 1 (and vice versa) in a Boolean expression.

Example: $A \cdot 0 = 0 \Rightarrow$ Dual: $A + 1 = 1$

4. **Compare half-adders and full-adders with truth tables and Boolean expressions.**

Half-Adder

Adds 2 bits

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A \cdot B$$

Full-Adder

Adds 3 bits (including carry)

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$

$$\text{Carry} = (A \cdot B) + (\text{Cin} \cdot (A \oplus B))$$

Truth table (Half-Adder):

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

5. **How do Karnaugh maps simplify Boolean expressions? Explain with steps.**

K-Maps simplify expressions by grouping 1s in adjacent cells. This removes redundant variables and gives the simplest form of the Boolean expression.

Steps:

- Draw K-map with required variables.
- Fill it using the truth table.
- Group adjacent 1s in sizes of 1, 2, 4, or 8.
- Write the simplified expression from the groups.

6. **Design a 4-bit binary adder using half and full adders.**

- Use 1 half-adder for the first bit.
- Use 3 full-adders for the remaining bits.
- Each full-adder takes a carry input from the previous stage.
- Draw circuit with connections and write Boolean expressions for each stage.

7. **Simplify the Boolean function using Boolean algebra rules:**

$$F(A, B) = A \cdot B + A \cdot B$$

Solution:

$$A \cdot B + A \cdot B = A (B + B) = A (1) = A$$

8. **Use De Morgan's laws to simplify the function:**

$$F(A, B, C) = A + B + AC$$

No negations here. But applying laws if needed:

If the expression were $\neg(A + B + AC)$, it becomes:

$$\neg A \cdot \neg B \cdot \neg A + \neg C$$

9. **Simplify the following expressions:**

(a) $A + B \cdot (A + B)$

Apply distributive:

$$A + A \cdot B + B \cdot B = A + A \cdot B + B = A + B$$

(b) $(A + B) \cdot (A + B)$

Same expression:

$$= A + B$$

(c) $A + A \cdot (B + C)$

Apply Absorption Law:

$$A + A \cdot X = A \Rightarrow A + A \cdot (B + C) = A$$

(d) $A \cdot B + A \cdot B$

$$= A \cdot (B + B) = A \cdot 1 = A$$

(e) $(A \cdot B) + (A \cdot B)$

$$= A \cdot (B + B) = A \cdot 1 = A$$